



Lab 2: **Testing of power devices** by Praprara Owodeha-Ashaka


Tetteh Bright

2nd February 2025

## Question 1

Use Fig.1 and DC sweep to obtain the I-V characteristics for the following diodes



a. Power rectifier Diode (**MUR460**)

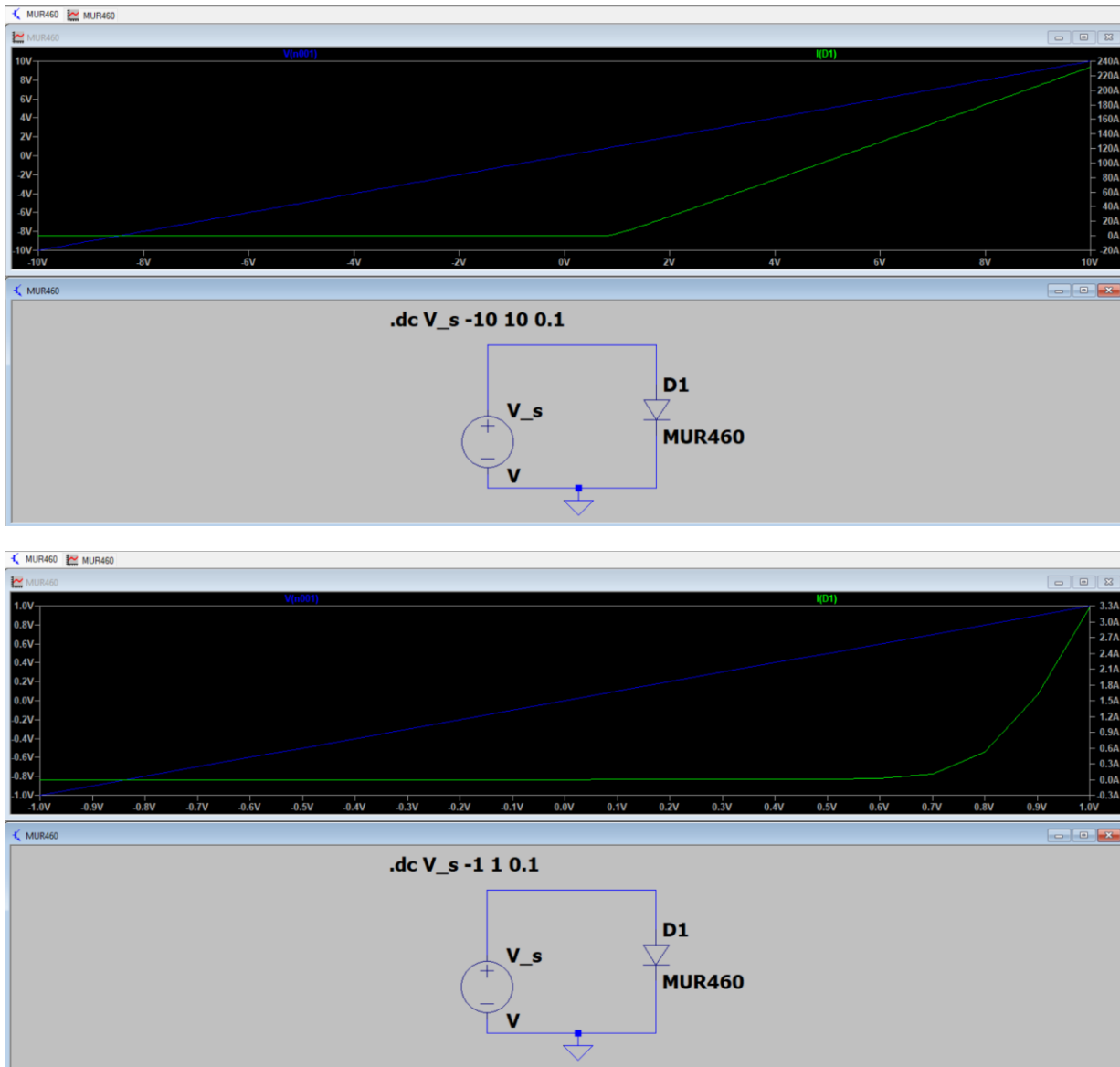


From this, we see that current through the diode is zero until the voltage across the diode exceeds a threshold (around 0.7 V), after which current starts to flow.

Zener diode (**DFLZ33**)


**.dc V\_s -100 100 0.1**

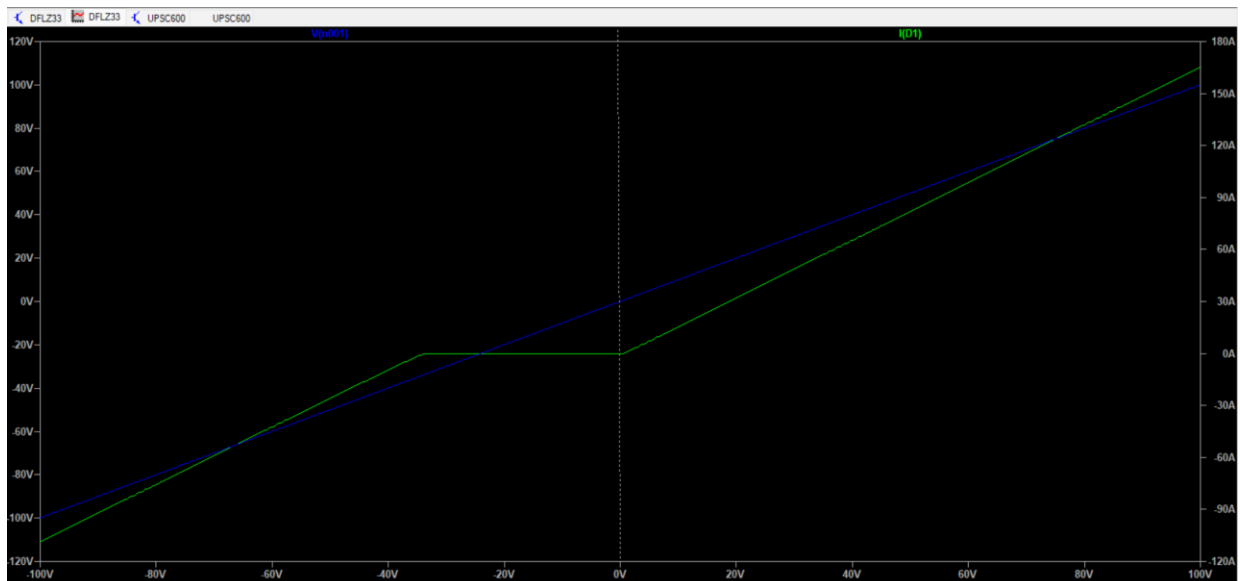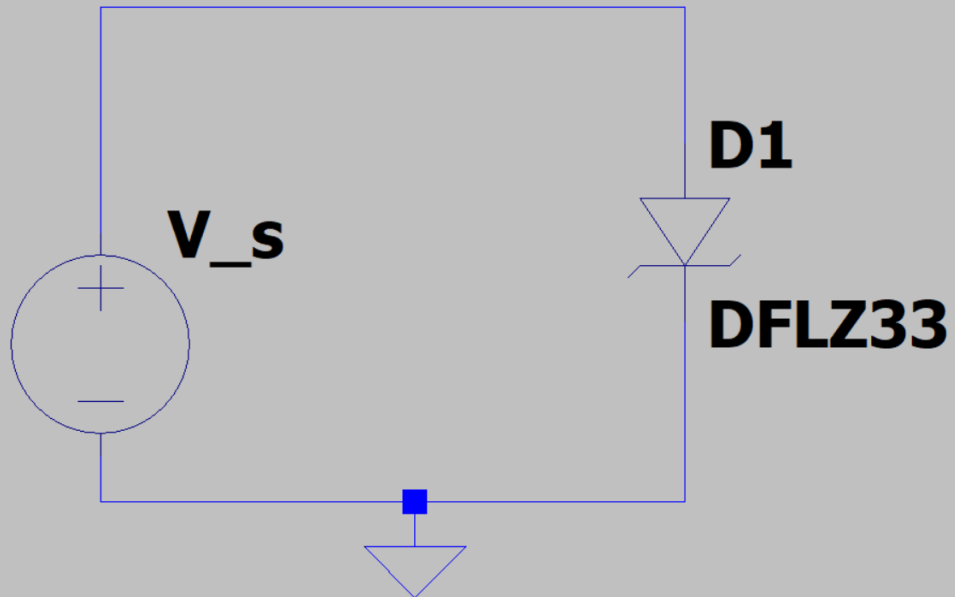


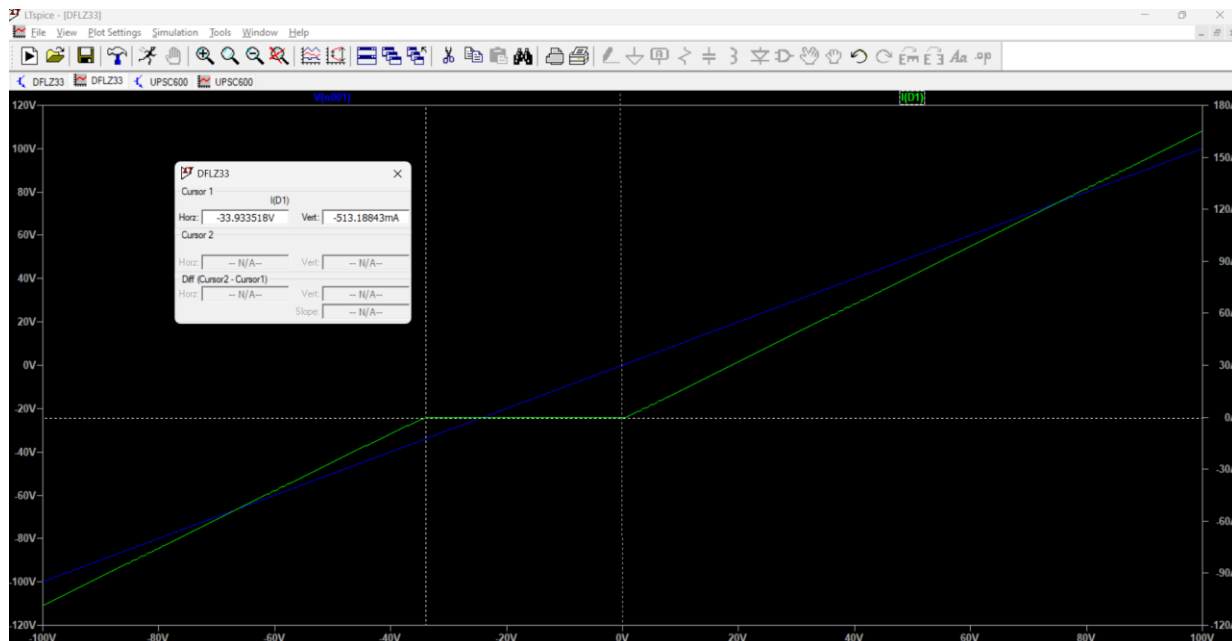

The Zener diode has a similar characteristic to the normal power diode when it is forward biased. When it is reverse biased, it restricts the flow of current until it gets to its Zener voltage range (31 to 35 volts), after which it allows flow of current in the reverse direction.



### Schottky diode (UPSC600)

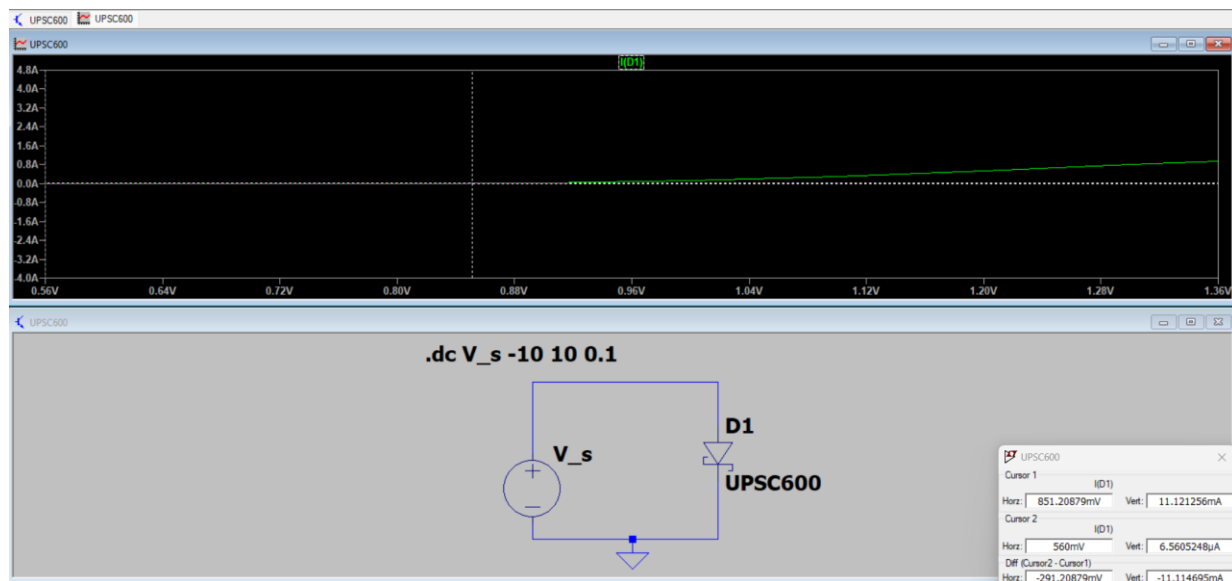

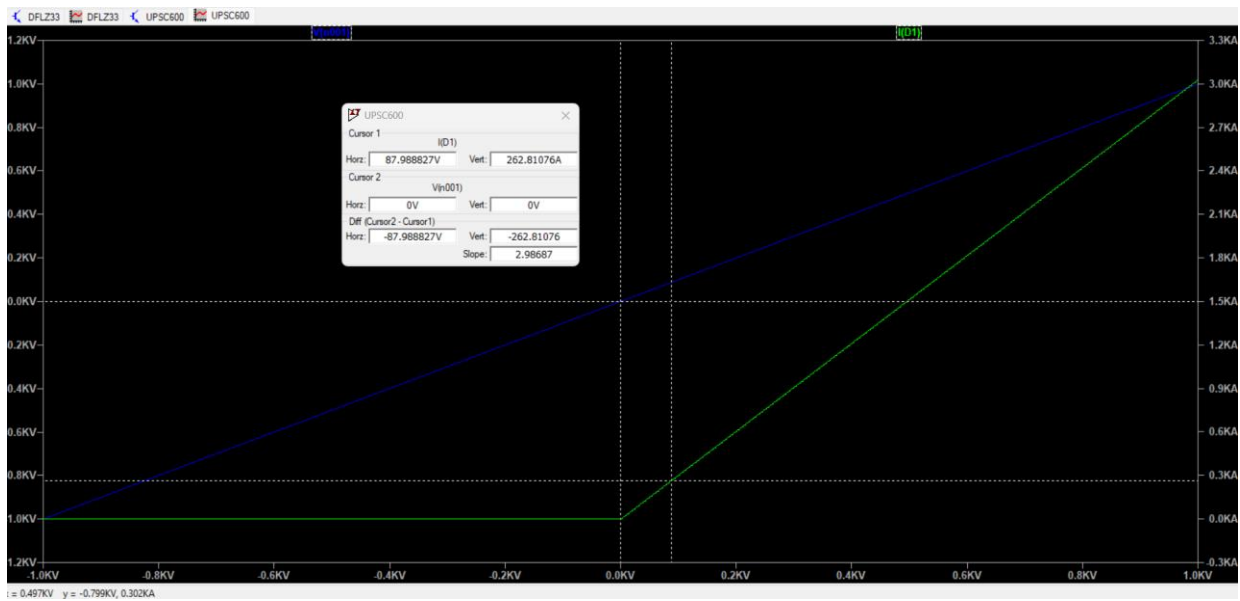

The schotky diode had a forward voltage drop less than the other two diodes (around 0.3 V). From the data sheet, the forward voltage drop is typically 1.6 V and from the simulation, the voltage drop is roughly 1 volt.


Number 2

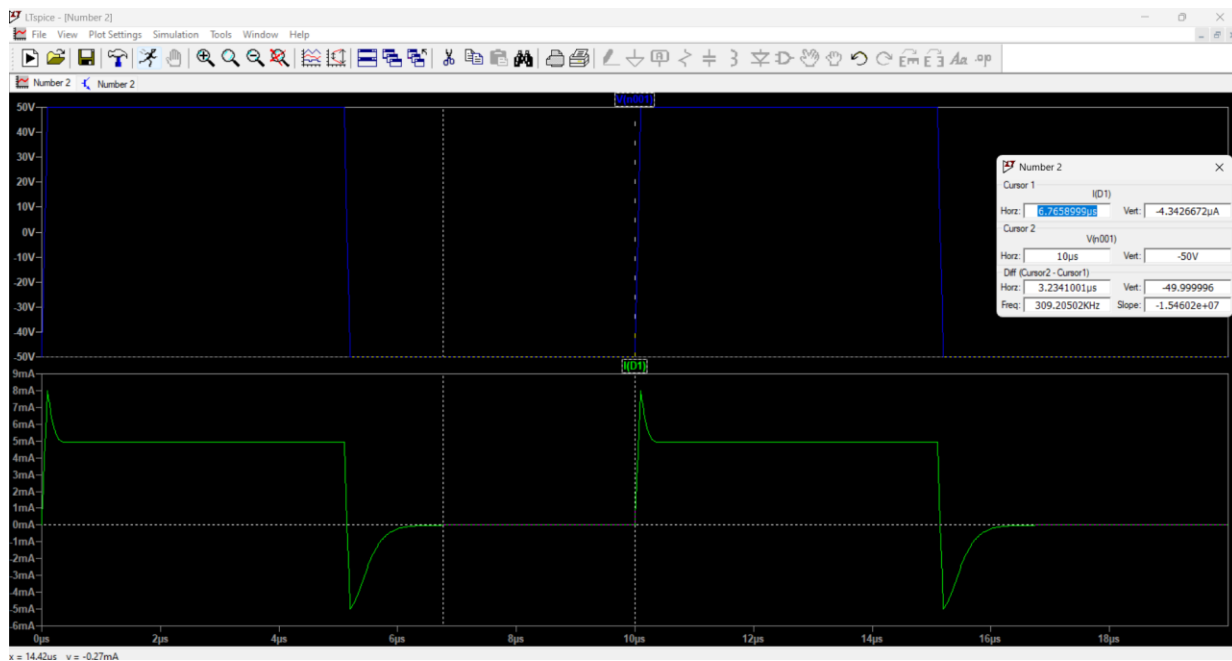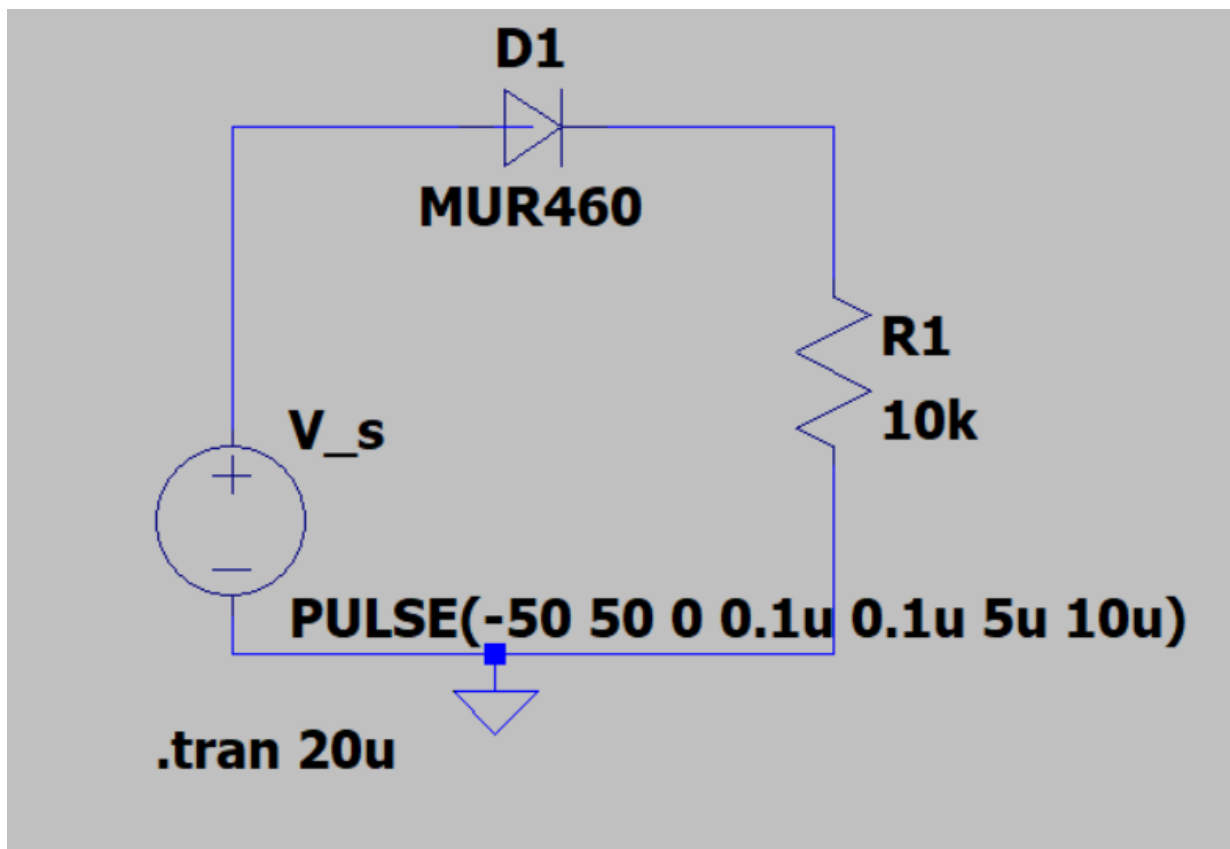

The time at 0 Amps for the first visible cycle is 5.147  $\mu$ s

The maximum negative is -4.89mA. 25% of this is -1.2245mA. The time at this 25% value is 5.656uA. Thus  $t_{rr} = 5.656 - 5.147 = 0.509 \text{ uS}$ . From the datasheet, the max reverse recovery time is 50 nS

### Number 3

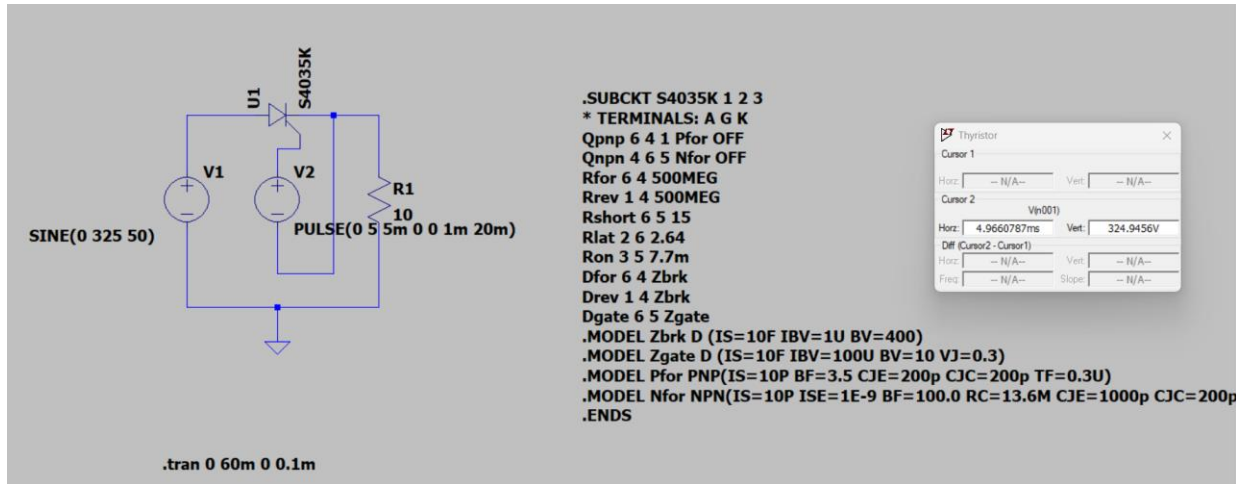


Main power source: 230 RMS, 50Hz. Period is 20m seconds

10 degrees:

Gate voltage:


Amplitude: 5 volts

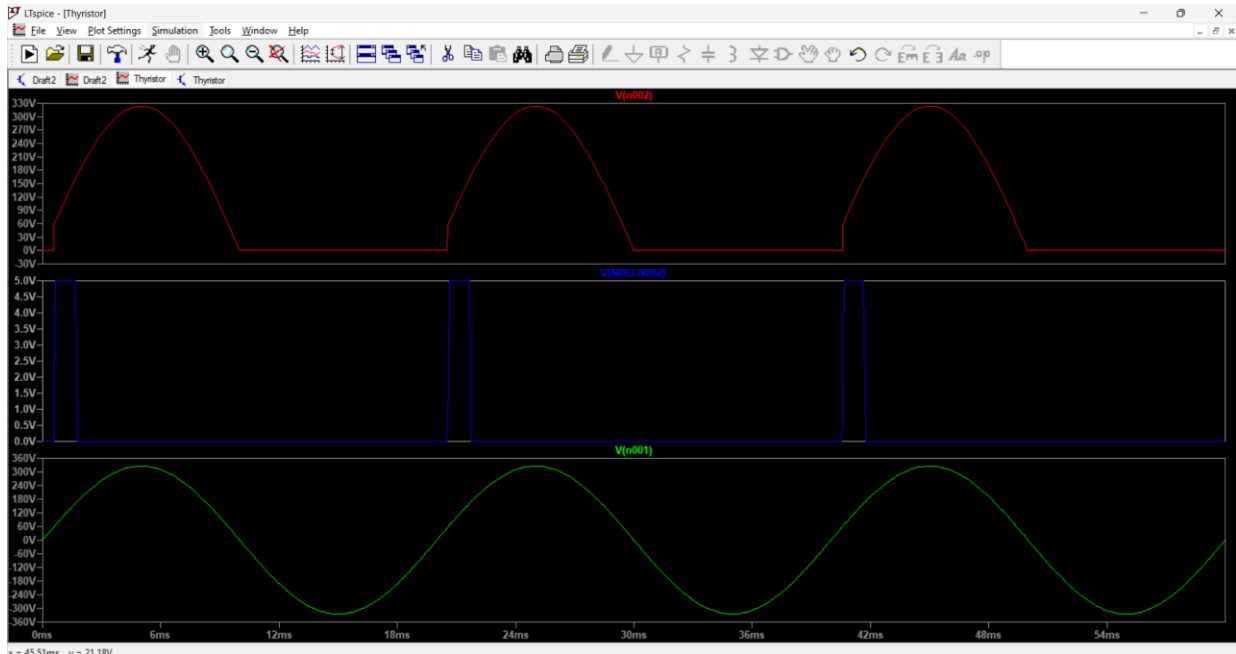T delay:  $(10/360)*20\text{m seconds} = 0.5556 \text{ mS}$




45 degrees

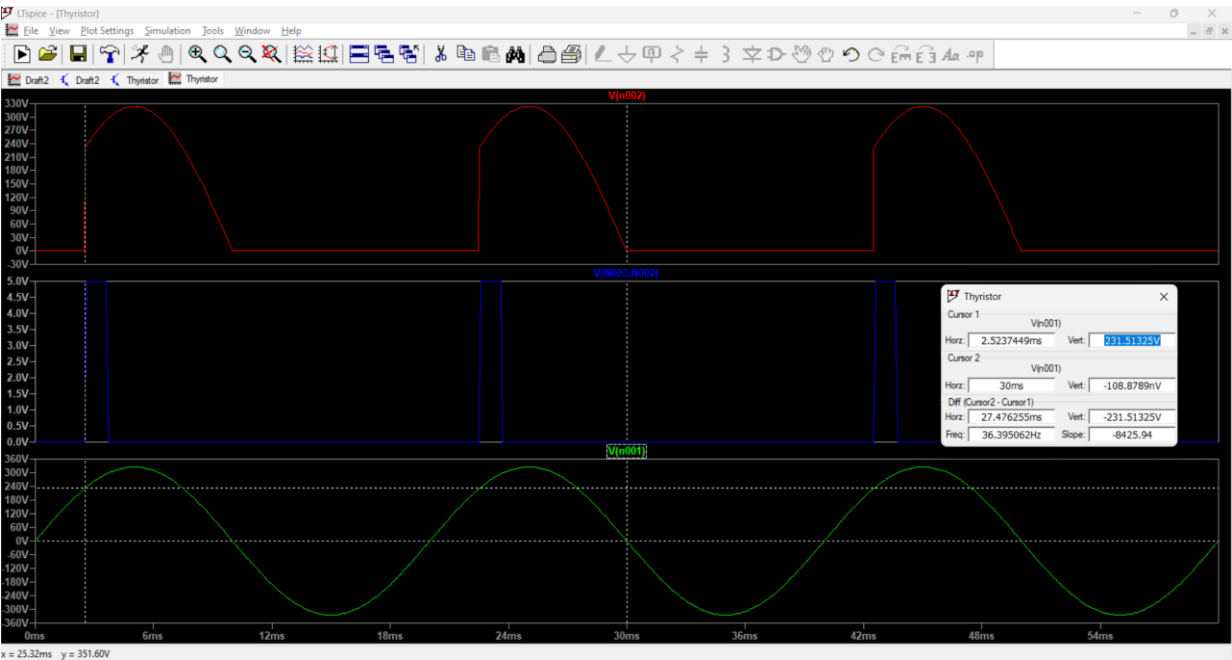$T \text{ delay: } (45/360) \cdot 20 \text{ ms} = 2.5 \text{ ms}$



90 degrees

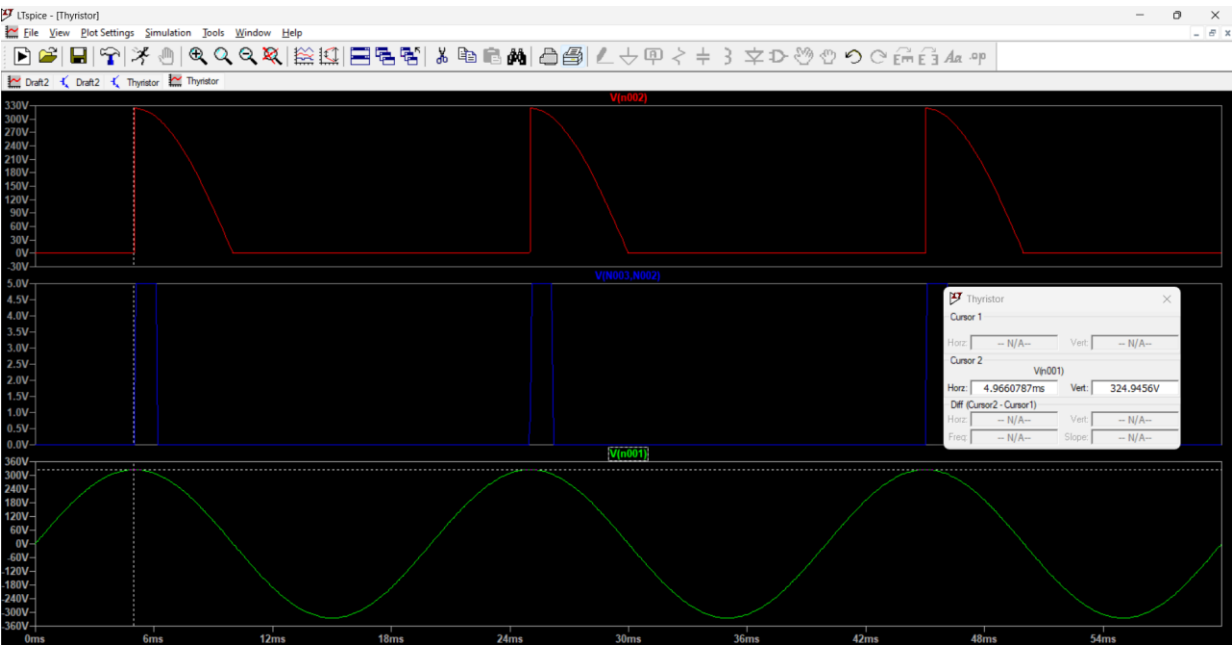$T \text{ delay: } (90/360) \cdot 20 \text{ ms} = 5 \text{ ms}$





The thyristor only gets powered on after the gate has been activated and it stays on throughout the positive cycle of the main circuit input voltage. In the negative cycle of the input voltage, the voltage output from the thyristor remains zero. Even though the circuit input voltage is in the positive cycle, the thyristor will not allow current to flow through it until the gate has been activated. The firing angle is the angle measured between when the thyristor becomes forward biased and when its gate gets activated. A smaller firing angle will lead to a greater average output per cycle.